

E12 Final Project:

Op Amps versus RLC Filters

Kevin Dee and Luke Pietrantonio

Introduction

Our goal in this project was to experiment with various filtering methods for radio communications. Our original goal was to create filters to pass 1.09 GHz ADS-B aircraft tracking signals.

Although theoretically possible, filtering at high frequencies was not easily realizable. We had more success filtering FM radio frequencies, around 90 MHz.

We attempted to compare a passive RLC series filter and an active Sallen-Key Op-Amp filter. We were unable to construct the RLC filter due to physical constraints, but the Op-Amp filter was successfully built.

Data Acquisition

Our data collection was done using an Airspy Mini USB device and Length v-dipole antenna


Filters were placed in-line, between the antenna and USB device

To analyze the data, we used SDRSharp (SDR#) and SpectrumSpy, both from Airspy



RLC Circuit

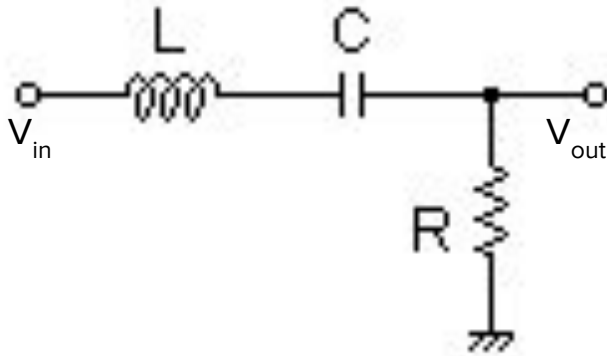
Our passive filter measures the voltage across the resistor of a series RLC circuit.



Op-Amp Circuit


Sallen-Key
Topology

- Simple
- Adds Gain

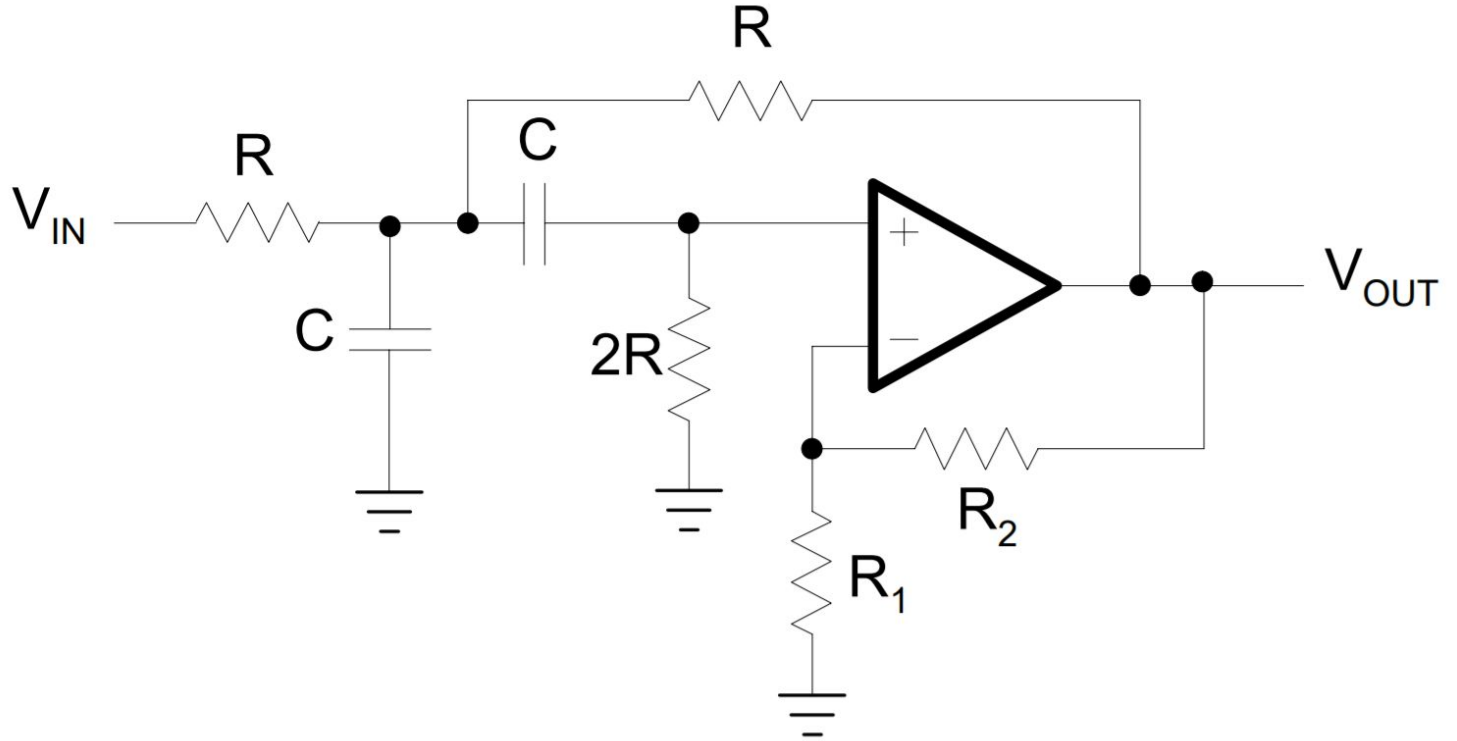

Theory: RLC

Basic RLC Bandpass Design

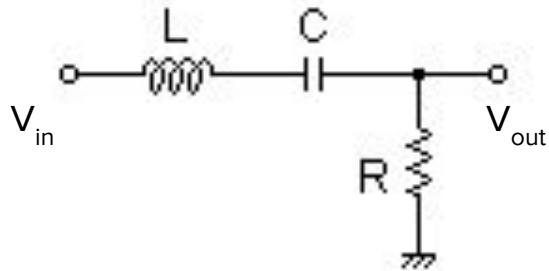

$$\frac{V_{out}}{V_{in}} = \frac{2\zeta(2\pi f_0)s}{s^2 + 2\zeta(2\pi f_0)s + (2\pi f_0)^2} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$Q = \frac{1}{2\zeta}$$

$$f_m = \frac{1}{2\pi\sqrt{LC}}$$

Sourced From Okawa Electric Design

Theory: RLC

Center Frequency: 97.75 MHz, the middle of the FM band

L = 10 μ H, the smallest inductor available

$$f_m = \frac{1}{2\pi\sqrt{LC}}$$

$$C = 0.265 \text{ pF}$$

Bandwidth: 20.5 MHz, to capture the entire FM band

$$Q = \frac{f_m}{\beta}$$

$$Q = 4.768$$

Theory: RLC

With $Q = 4.768$

$$Q = \frac{1}{2\zeta}$$


$$\zeta = 0.104866$$

Calculate value of R

$$2\zeta(2\pi f_0)s = \frac{R}{L}s$$

$$R = 1.288 \text{ k}\Omega$$

Theoretical: RLC Circuit

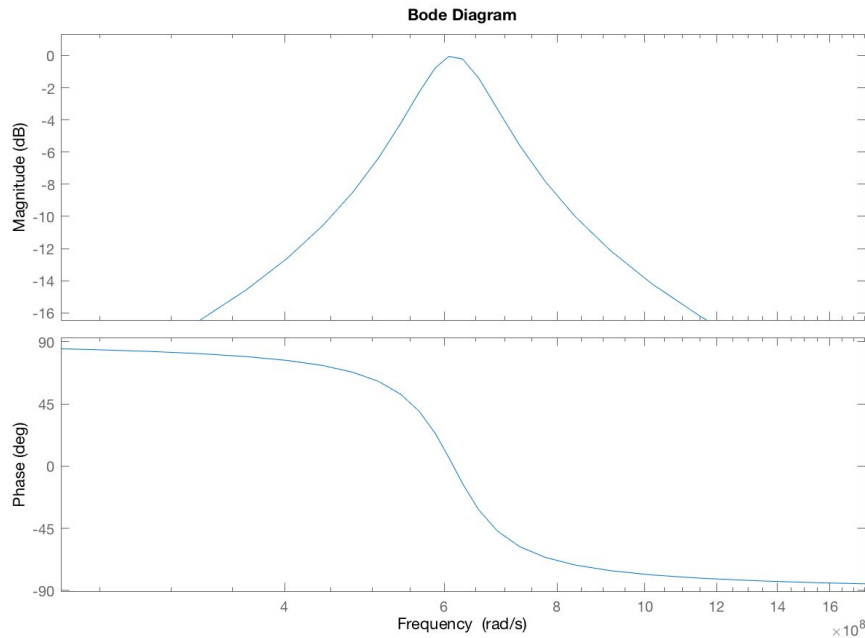


$$H(s) = \frac{1.288e08 s}{s^2 + 1.288e08 s + 3.774e17}$$

- Steeper magnitude change than OP Amp filter
- Magnitude of peak at 0, due to lack of amplification
- Peak is centered near the targeted frequency

Theory: OP Amp

Sallen-Key Design:

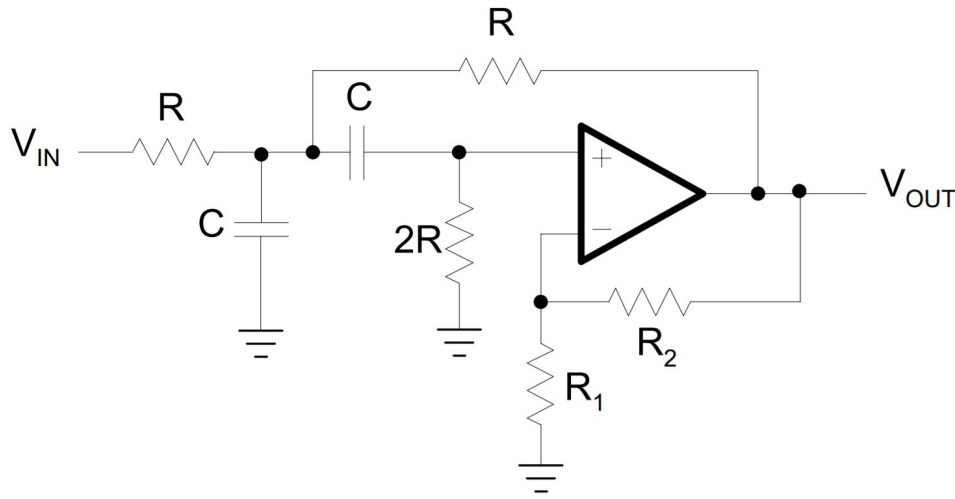

$$f_m = \frac{1}{2\pi RC}$$

$$Q = \frac{f_m}{\beta} \quad Q = \frac{1}{3 - G}$$

$$G = 1 + \frac{R_2}{R_1}$$

$$A_m = \frac{G}{3 - G}$$

Sourced from *Op-Amps for Everyone* (2002) Texas Instruments

Theory: OP Amp

Center Frequency: 97.75 MHz, the middle of the FM band

C = 5 pF, the smallest capacitor available

$$f_m = \frac{1}{2\pi RC}$$

$$R = 326 \Omega$$

Bandwidth: 20.5 MHz, to capture the entire FM band

$$Q = \frac{f_m}{\beta}$$

$$Q = 4.768$$

Theory: OP Amp

From $Q=4.768$, gain and amplification at center frequency can be calculated

$$Q = \frac{1}{3 - G}$$

$$G=2.8$$

$$A_m = \frac{G}{3 - G}$$

$$A_m = 14$$


$$G = 1 + \frac{R_2}{R_1}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1.8 \text{ k}\Omega$$

Observations v. Theoretical: Op-Amp



Bode Diagram

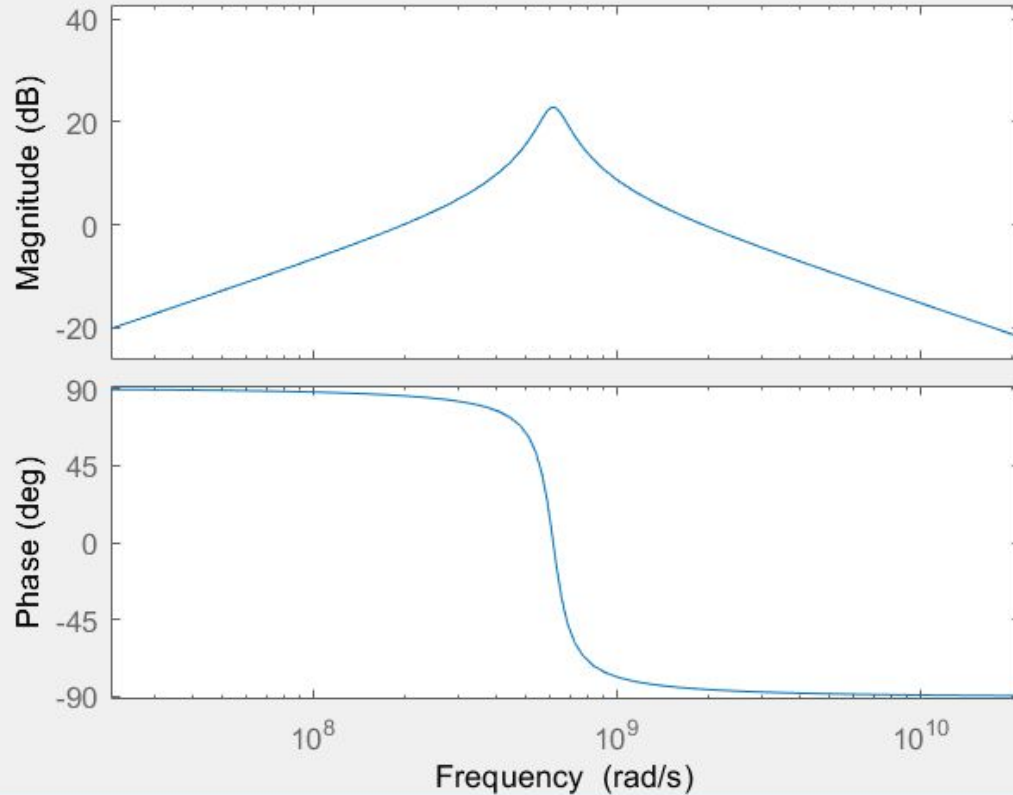

$$H(s) = \frac{1.718e09 s}{s^2 + 1.227e08 s + 3.764e17}$$

- Magnitude is greater than 0 at the peak
- Peak width is 20.5 Mhz to accommodate the entire FM band

Observations v. Theoretical: Op-Amp

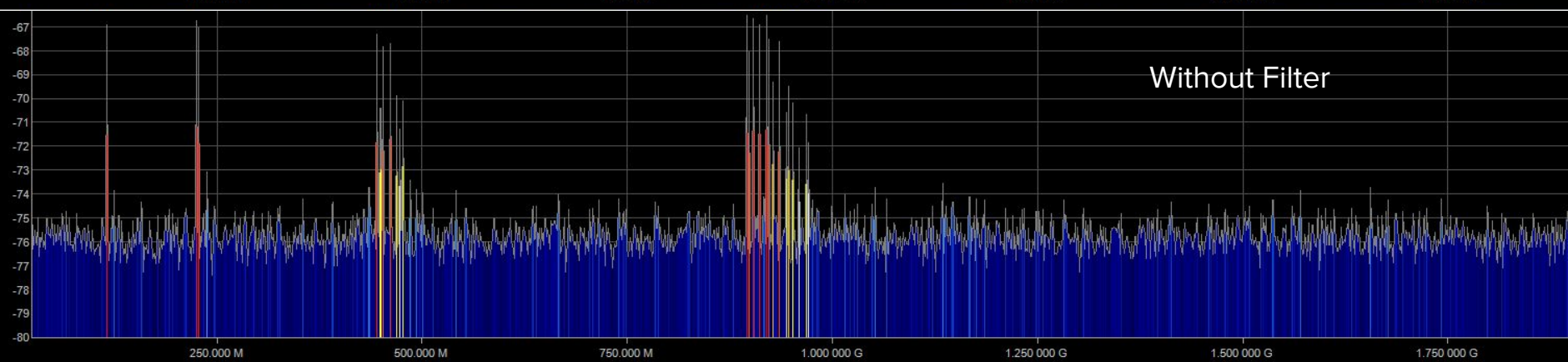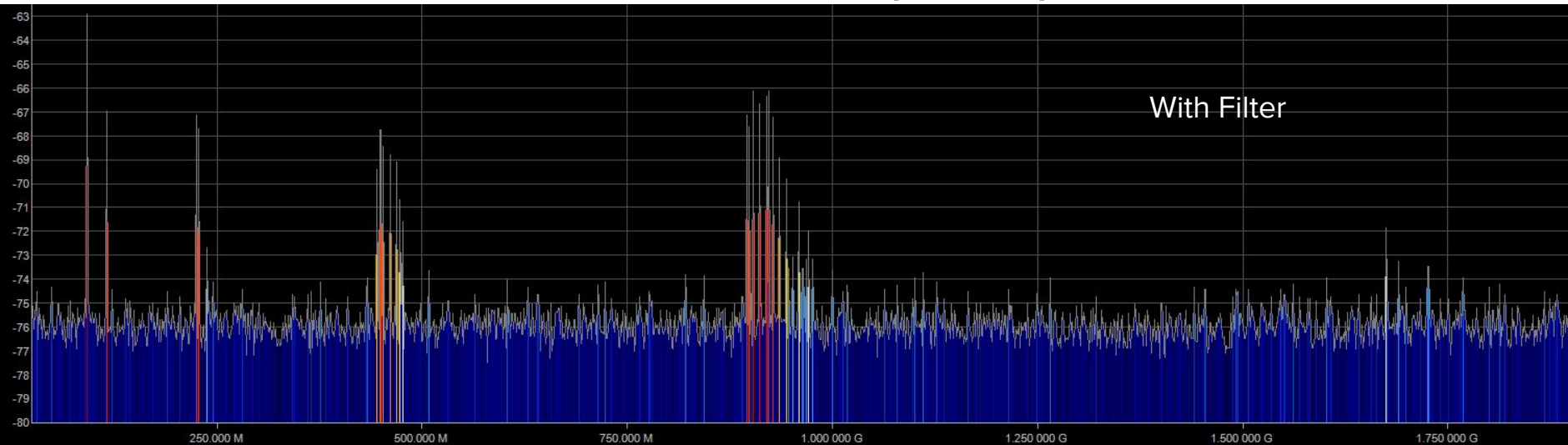

Summary

RLC Bandpass not physically realizable

$$C = 0.265 \text{ pF}$$

Attempted to make, but would have required too many capacitors in series

OP Amp Bandpass was physically realizable

Did not successfully filter

Amplified our desired band

Conclusion

The original goal of making a 1.09 GHz filter for receiving ADS-B aircraft tracking signals was not realizable.

Lower frequency filtering was possible for an active filter, but not for a passive filter.

The filter did not successfully block signals outside of the pass band, but it did amplify those within.

To remedy this, proper RF shielding would be necessary.